

Analog-to-Digital Converter (ADC)

Embedded System 2561, KU CSC

Adapted by Sorayut Glomglome

Outline

1. Analog-to-Digital Conversion
2. Keywords
3. ADC Applications
4. Nyquist Sampling Theorem
5. ADC architecture
6. STM32F411 ADC Module

Learning Outcomes

1. Understanding analog-to-digital conversion
2. Using analog input with MCU
3. Reading analog-to-digital data

Analog-to-Digital Conversion : Terminology

Analog : continuously valued signal, such as temperature or speed, with infinite possible values in between


Digital : discretely valued signal, such as integers, encoded in binary

analog-to-digital converter: ADC, A/D, A2D; converts an analog signal to a digital signal

digital-to-analog converter: DAC, D/A, D2A

An embedded system's surroundings typically involve many analog signals.

Analog-to-Digital Converter

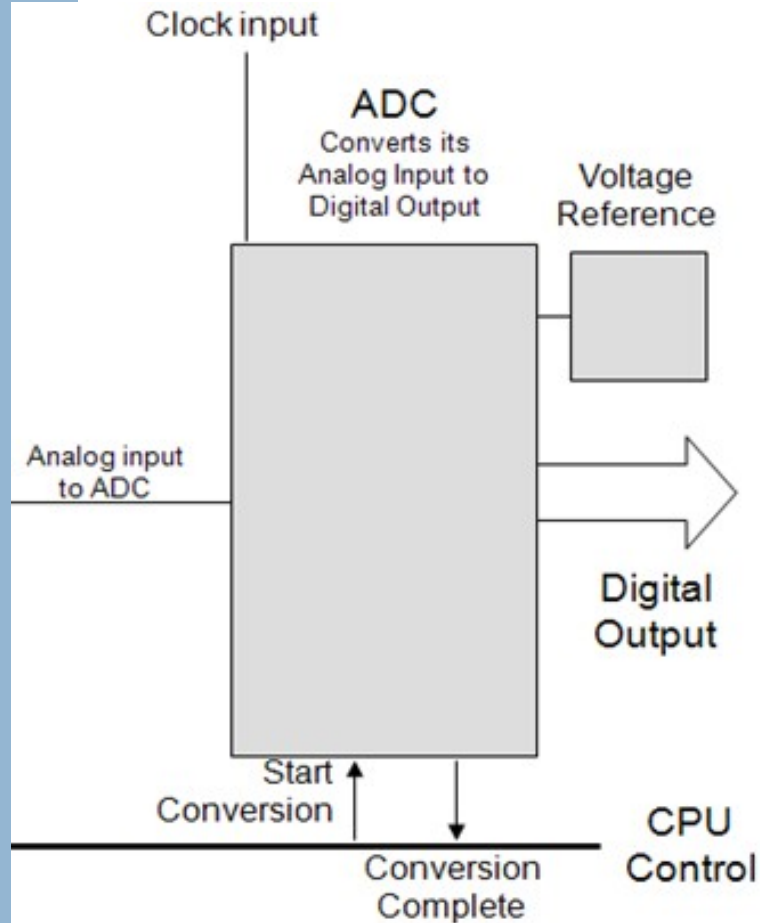


- ADC is an electronic circuit that **measures the input voltage**, and gives a binary output number **proportional** to its size.
- ADC compares an input voltage to a **reference voltage**.
- Conversion takes **time ($\mu s++$)**, so the ADC needs to **signal** when it has finished.

Analog-to-digital converters

$V_{\max} = 7.5V$


7.5V	1111
7.0V	1110
6.5V	1101
6.0V	1100
5.5V	1011
5.0V	1010
4.5V	1001
4.0V	1000
3.5V	0111
3.0V	0110
2.5V	0101
2.0V	0100
1.5V	0011
1.0V	0010
0.5V	0001
0V	0000

proportionality

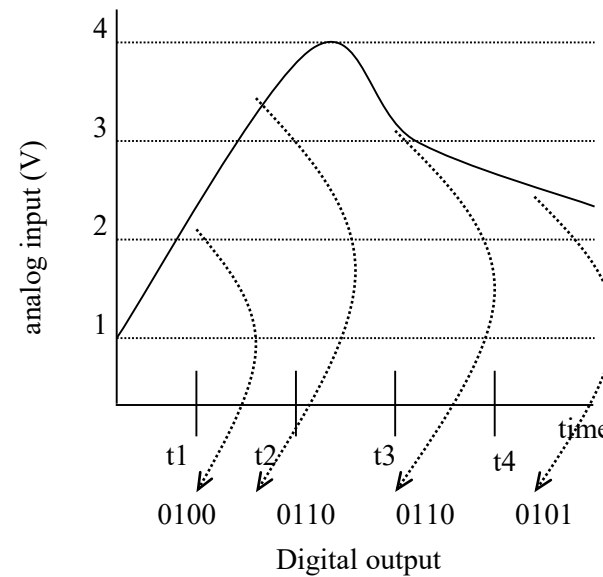

analog to digital

Range, Resolution and Quantisation

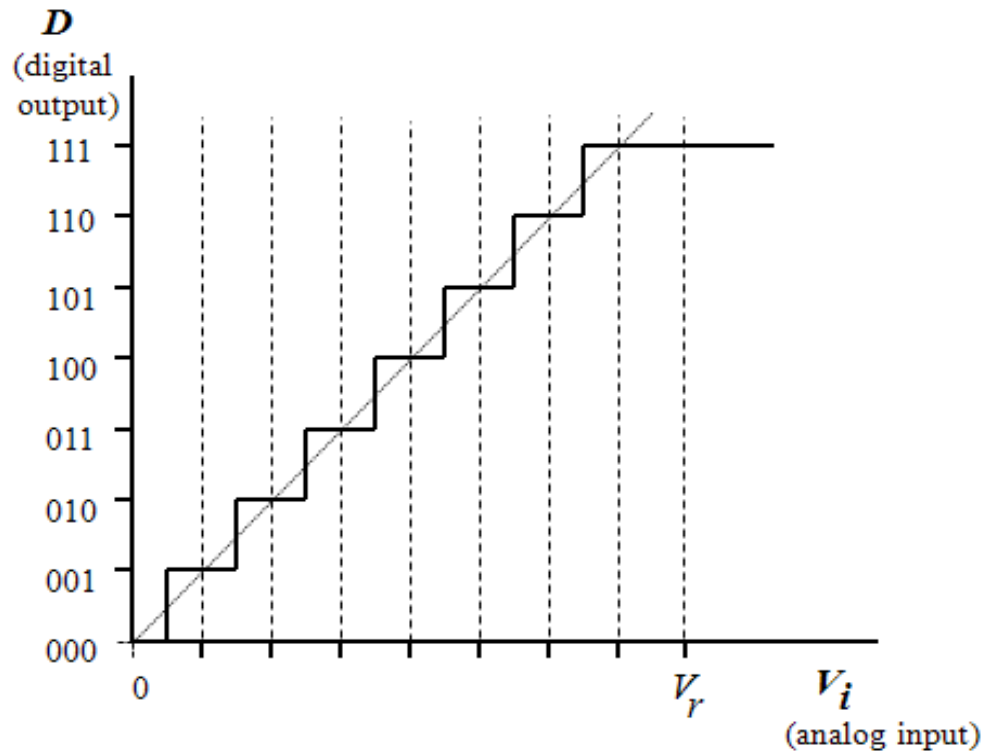

$$D = \frac{V_i}{V_r} \times 2^n$$

- The ADC action follows Equation
 - D : output binary number
 - n : bit number
 - V_i : input voltage
 - V_r : reference voltage
- The difference between the maximum and minimum input values is called the Range.
- many ADC circuits the range is equal to the reference voltage.

Proportional Signals

Simple Equation

Assume minimum voltage of 0 V.

V_{max} = maximum voltage of the analog signal

a = analog value


n = number of bits for digital encoding

2^n = number of digital codes

M = number of steps, either 2^n or $2^n - 1$

d = digital encoding

$$a / V_{max} = d / M$$

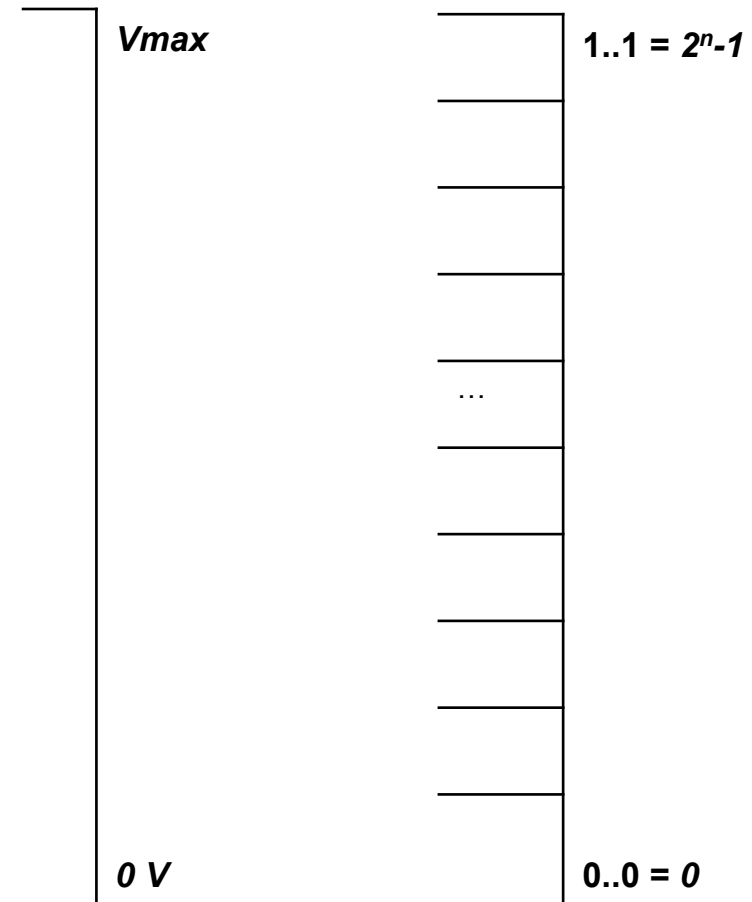

Resolution

Let $n = 2$

$$\underline{M = 2^n - 1}$$

3 steps on the digital scale

$$d_0 = 0 = 0b00$$

$$d_{V_{max}} = 3 = 0b11$$


$$\underline{M = 2^n}$$

4 steps on the digital scale

$$d_0 = 0 = 0b00$$

$$d_{V_{max} - r} = 3 = 0b11 \text{ (no } d_{V_{max}} \text{)}$$

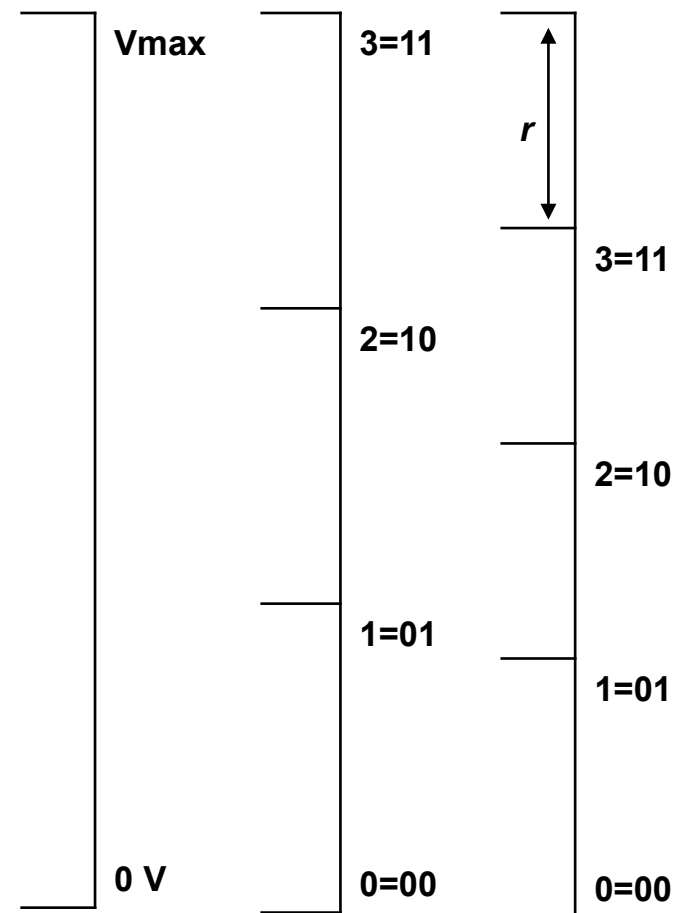r , resolution: smallest analog change resulting from changing one bit



Resolution


ADC: V_{in} = input voltage, V_{ref} = reference voltage

N = number of bits of precision

$$V_{in} / V_{ref} * 2^N = \text{output_code}$$

$$\text{output_code} / 2^N * V_{ref} = V_{in}$$

$$1 \text{ LSB} = V_{ref} / 2^N$$

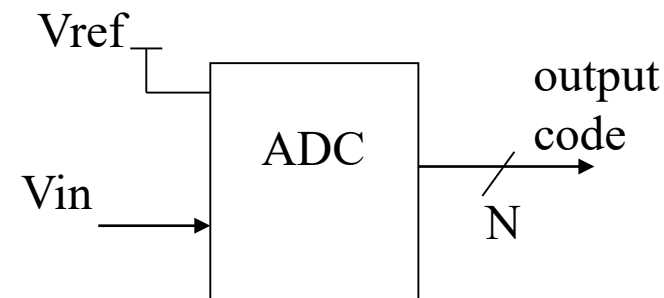


DAC: V_{out} = output voltage, V_{ref} = reference voltage,

N = number of bits of precision

$$V_{out} / V_{ref} * 2^N = \text{input_code}$$

$$\text{input_code} / 2^N * V_{ref} = V_{out}$$


$$1 \text{ LSB} = V_{ref} / 2^N$$

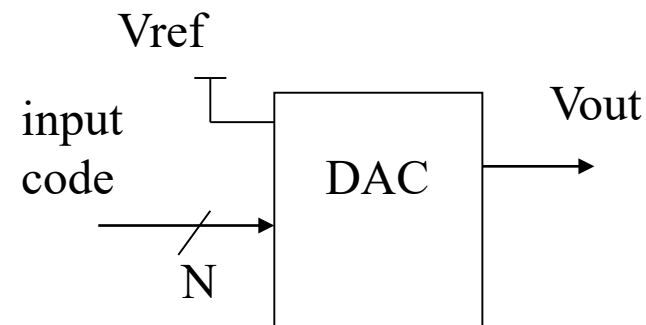


ADC Applications

- Data logging
- Audio
 - Speech recognition
 - special effects (reverb, noise cancellation, etc)
- Video
 - Filtering
 - Special effects
 - Compression


Digital Signal Processing

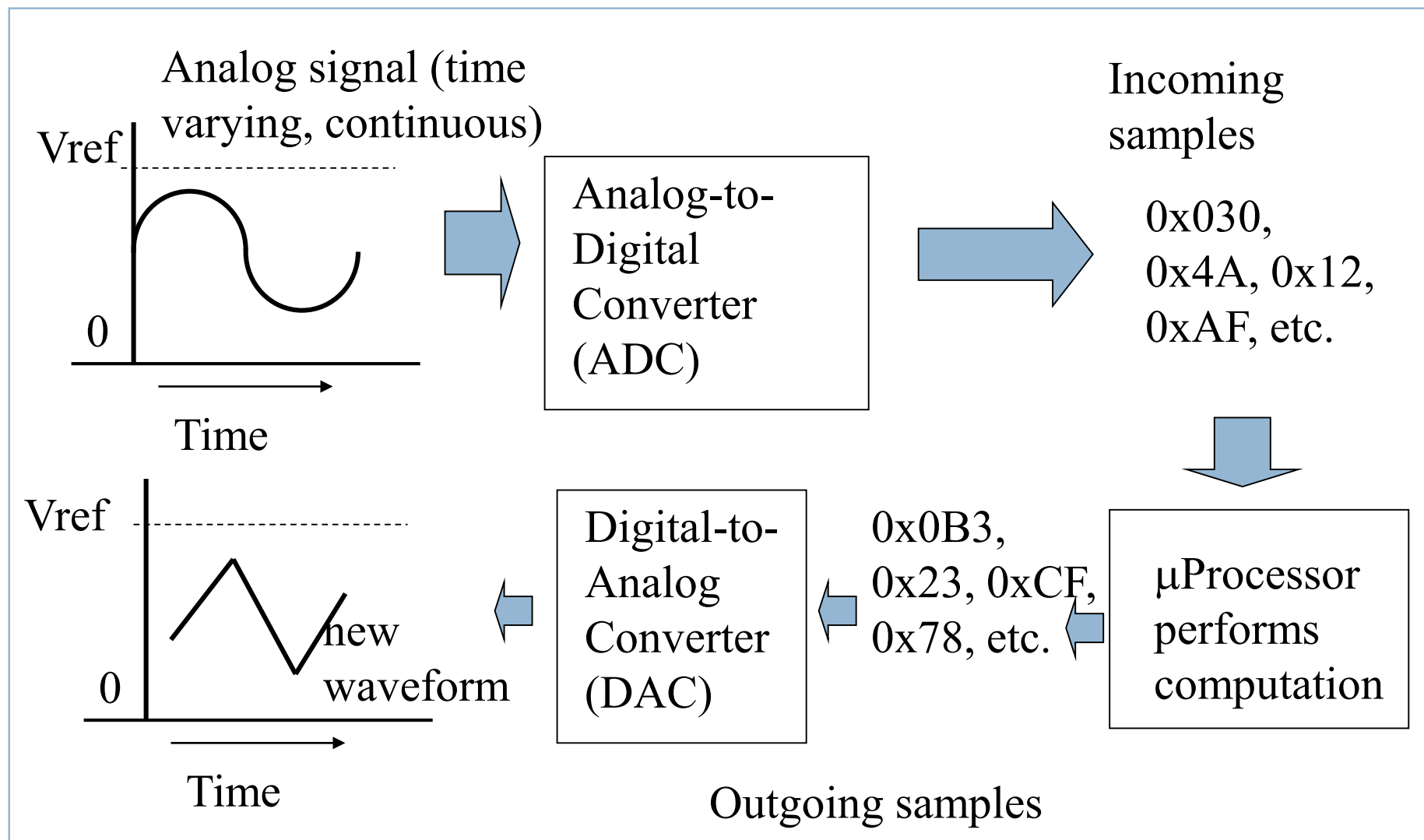

Sampling Frequency and Aliasing

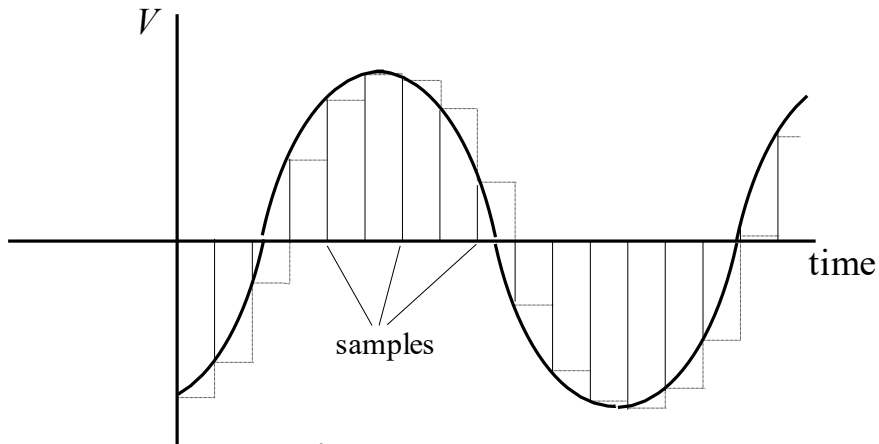

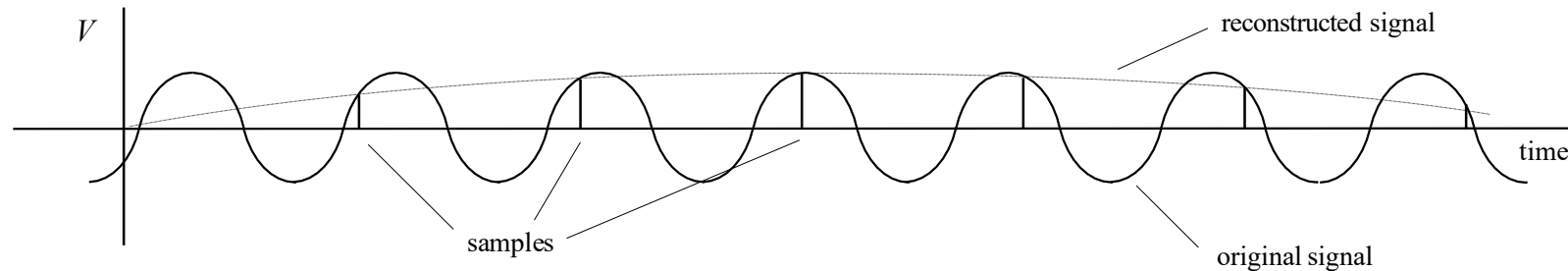
- Sample and quantise
- More samples more accurate the digital data
- sampling frequency



The Nyquist theorem (sampling theorem):

- Sampling frequency must be at least twice of the maximum signal frequency.
- If the sampling is less than twice, then *aliasing* occurs
- Aliasing : a new lower frequency signal.

Aliasing of Two Sinewaves

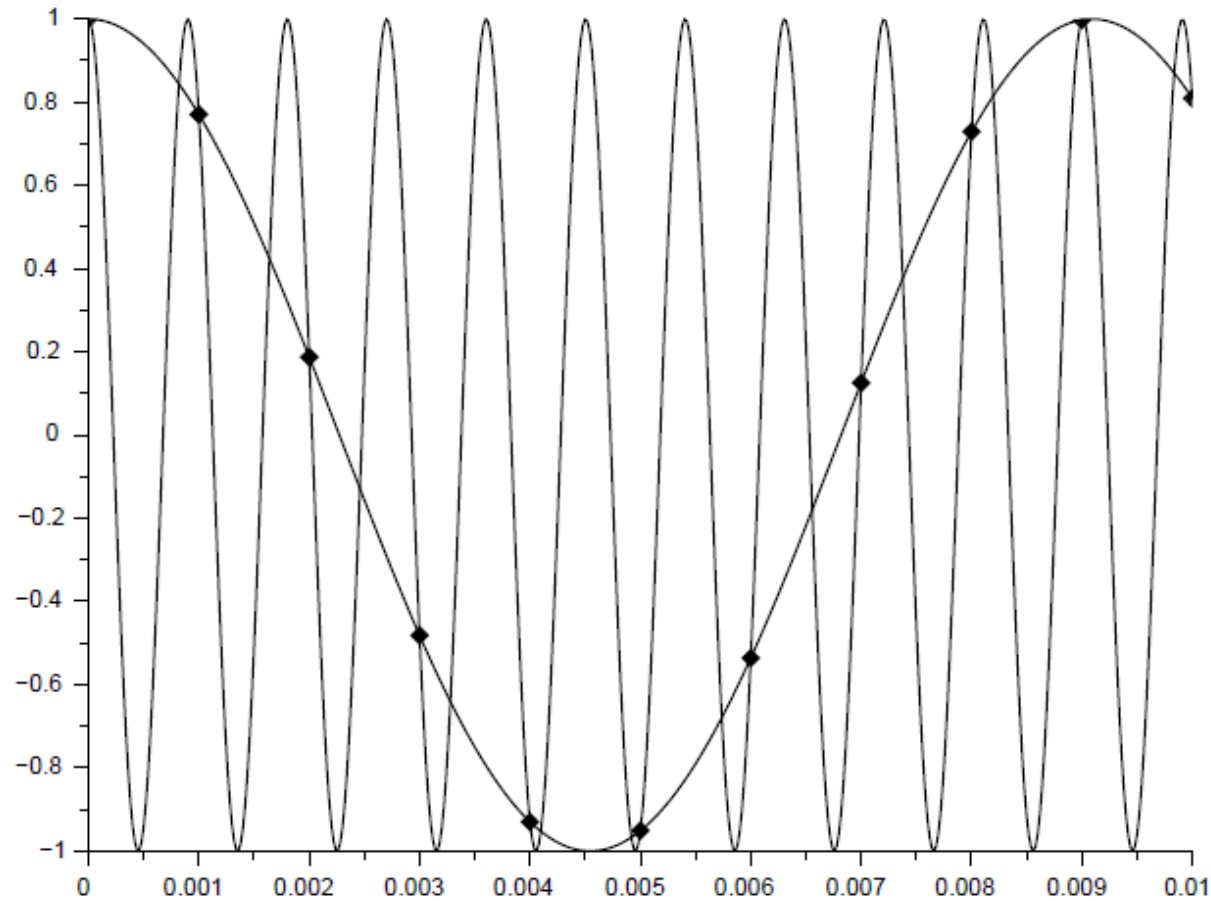

Sample ADC Computations

If $V_{ref} = 5V$, and the 10-bit A/D output code is 0x12A, what is the ADC input voltage?

$$\begin{aligned} \text{output_code}/2^N * V_{ref} &= (0x12A)/2^{10} * 5 \text{ V} \\ &= 298/1024 * 5 \text{ V} = 1.46 \text{ V (Vin)} \end{aligned}$$


If $V_{ref} = 5V$, and the upper 8 bits of the A/D output code is 0xA9, what is the ADC input voltage?

$$\begin{aligned} \text{output_code}/2^N * V_{ref} &= (0xA9)/2^8 * 5 \text{ V} \\ &= 169/256 * 5 \text{ V} = 3.3 \text{ V (Vin)} \end{aligned}$$


If $V_{ref} = 4V$, and the A/D input voltage is 2.35 V, what is the ADC output code, upper 8-bits?

$$\begin{aligned} V_{in}/V_{ref} * 2^N &= 2.35 \text{ V} / 4 \text{ V} * 2^8 \\ &= .5875 * 256 = 150.4 = 150 = 0x96 \end{aligned}$$

A 1-bit ADC

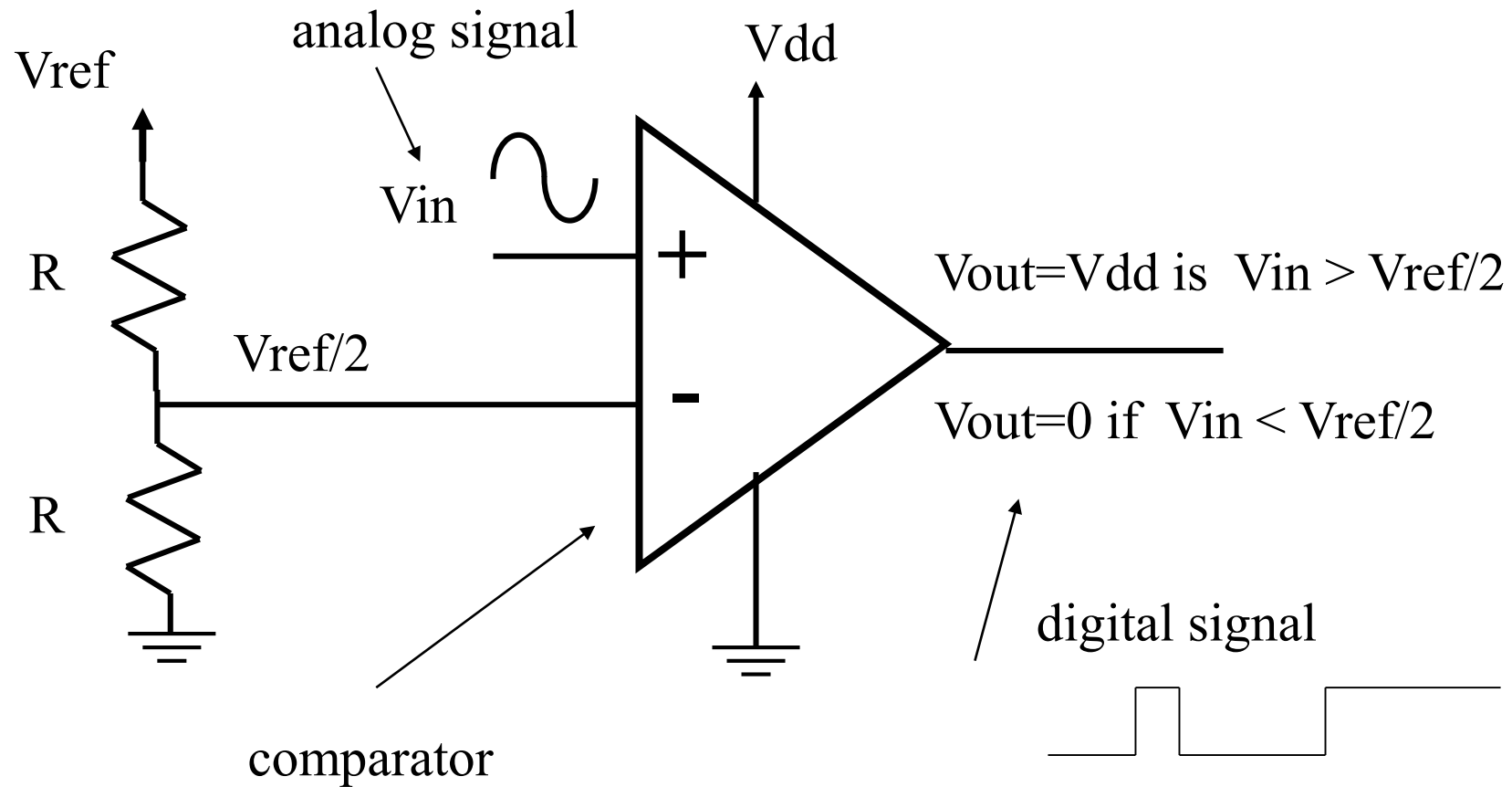


A 2-bit ADC

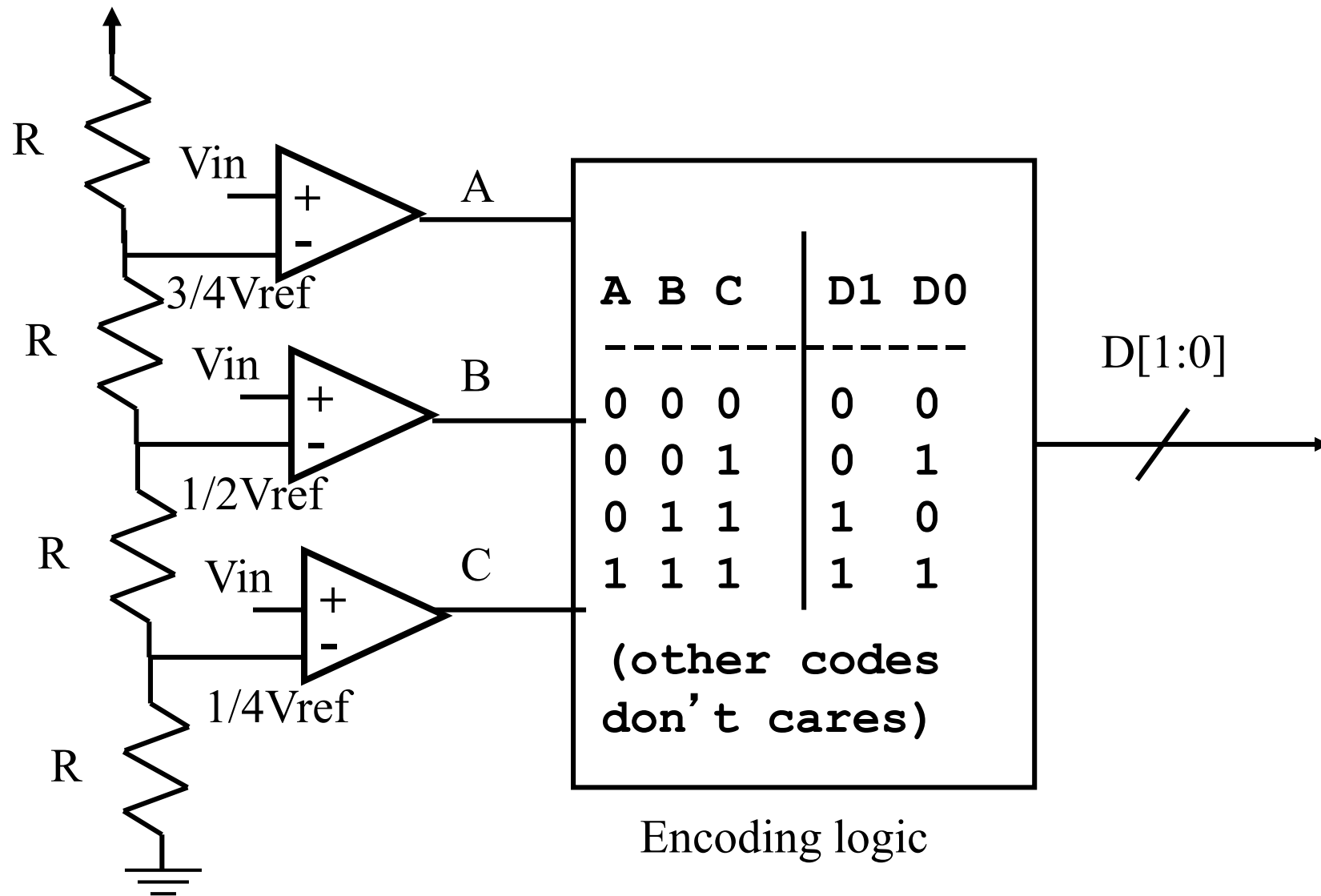

ADC Architectures

- The previous architectures are called *Flash* ADCs
 - Fastest possible conversion time
 - Requires the most transistors of any architecture
 - N-bit converter requires 2^N-1 comparators.
 - Commercially available flash converters up to 12 bits.
 - Conversion done in one clock cycle
- *Successive approximation* ADCs
 - Use only one comparator
 - Take one clock cycle per bit
 - High precision (16-bit converters are available)

Successive Approximation ADC

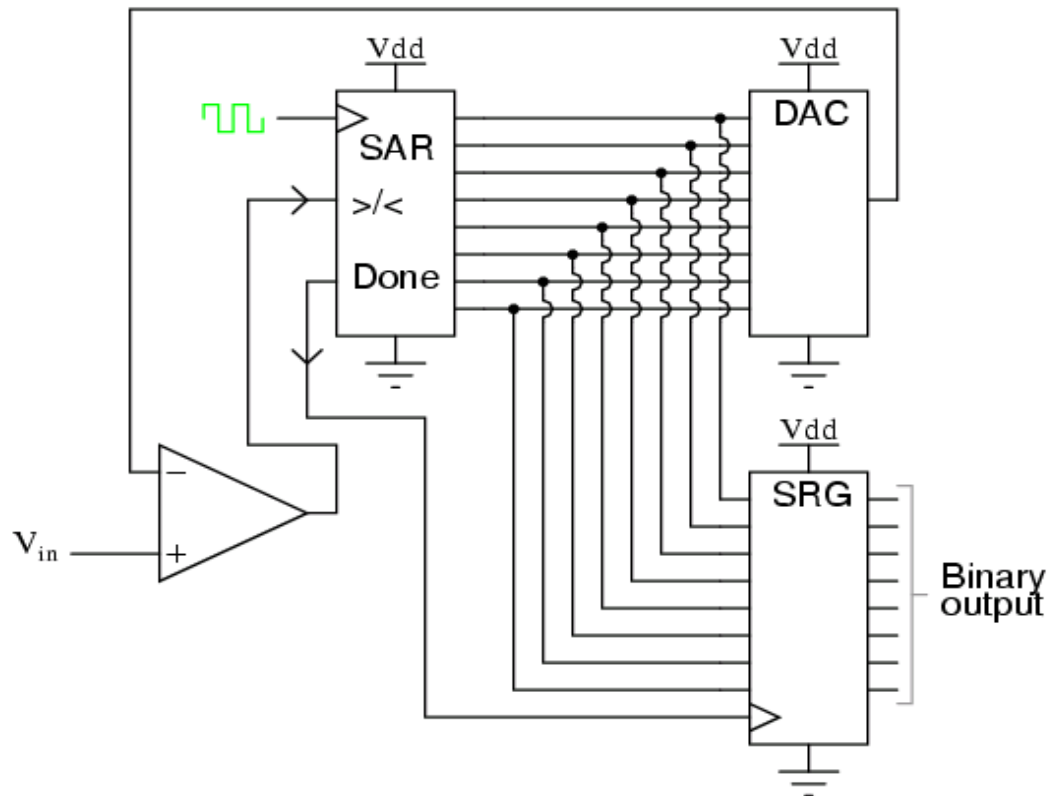

Output is Q[N]

First, set DAC to produce $V_{ref}/2$.

Output of Comparator is Q[N-1] (MSB)

If MSB = 1, then V_{in} between V_{ref} and $V_{ref}/2$, so set DAC to produce $3/4 V_{ref}$.

If MSB=0, then V_{in} between $V_{ref}/2$ and 0, so set DAC to $1/2 V_{ref}$.

Output of comparator is now Q[N-2].

Do this for each bit.

Takes N cycles.

ADC using successive approximation

- Given an analog input signal whose voltage should range from 0 to 15 volts, and an 8-bit digital encoding, calculate the correct encoding for 5 volts. Then trace the successive-approximation approach to find the correct encoding.
- Assume $M = 2^n - 1$

$$a / V_{max} = d / M$$

$$5 / 15 = d / (256 - 1)$$

$$d = 85 \text{ or binary } 01010101$$

ADC using successive approximation

Step 1-4: determine bits 0-3

$$\frac{1}{2}(V_{max} - V_{min}) = 7.5 \text{ volts}$$
$$V_{max} = 7.5 \text{ volts.}$$

0	0	0	0	0	0	0	0
---	---	---	---	---	---	---	---

$$\frac{1}{2}(7.5 + 0) = 3.75 \text{ volts}$$
$$V_{min} = 3.75 \text{ volts.}$$

0	1	0	0	0	0	0	0
---	---	---	---	---	---	---	---

$$\frac{1}{2}(7.5 + 3.75) = 5.63 \text{ volts}$$
$$V_{max} = 5.63 \text{ volts}$$

0	1	0	0	0	0	0	0
---	---	---	---	---	---	---	---

$$\frac{1}{2}(5.63 + 3.75) = 4.69 \text{ volts}$$
$$V_{min} = 4.69 \text{ volts.}$$

0	1	0	1	0	0	0	0
---	---	---	---	---	---	---	---

ADC using successive approximation

Step 5-8: Determine bits 4-7

$$\frac{1}{2}(5.63 + 4.69) = 5.16 \text{ volts}$$
$$V_{max} = 5.16 \text{ volts.}$$

0	1	0	1	0	0	0	0
---	---	---	---	---	---	---	---

$$\frac{1}{2}(5.16 + 4.69) = 4.93 \text{ volts}$$
$$V_{min} = 4.93 \text{ volts.}$$

0	1	0	1	0	1	0	0
---	---	---	---	---	---	---	---


$$\frac{1}{2}(5.16 + 4.93) = 5.05 \text{ volts}$$
$$V_{max} = 5.05 \text{ volts.}$$

0	1	0	1	0	1	0	0
---	---	---	---	---	---	---	---

$$\frac{1}{2}(5.05 + 4.93) =$$
$$4.99 \text{ volts}$$

0	1	0	1	0	1	0	1
---	---	---	---	---	---	---	---

Constructing ADC

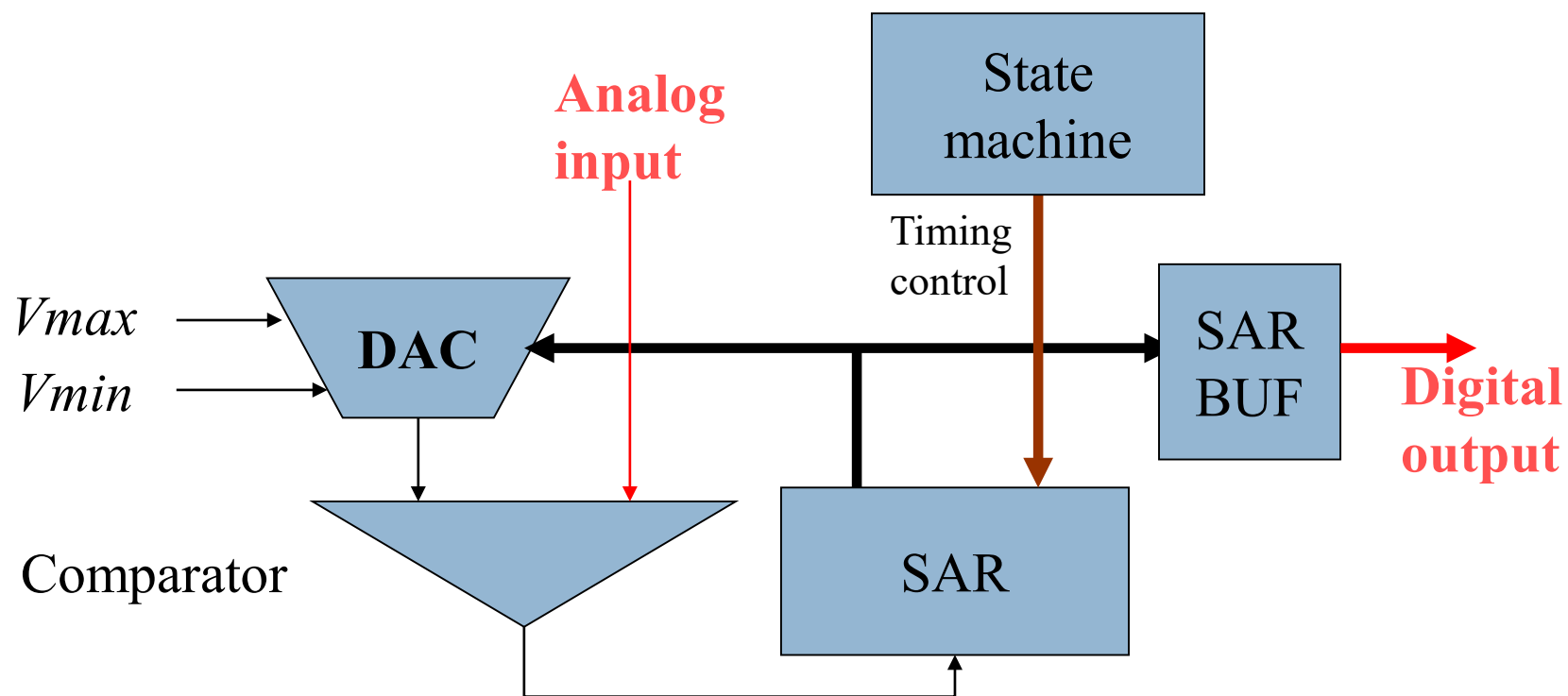

SAR: Successive
approximation register

STM32F411 ADC Module

- 12-bit ADC is a successive approximation analog-to-digital converter
- A/D conversion of the channels can be performed in single, continuous, scan or discontinuous mode.
- The result of the ADC is stored into a left or right-aligned 16-bit data register.

STM32F411 ADC Features

- 12-bit, 10-bit, 8-bit or 6-bit configurable resolution
- Interrupt generation at the end of conversion
- Single and continuous conversion modes
- Regular and Injection mode
- Data alignment with in-built data coherency
- ADC supply requirements: 2.4 V to 3.6 V at full speed and down to 1.8 V at slower speed
- ADC input range: $V_{REF-} \leq V_{IN} \leq V_{REF+}$

Examples of Conversion Mode

Figure 4. Single-channel, continuous conversion mode



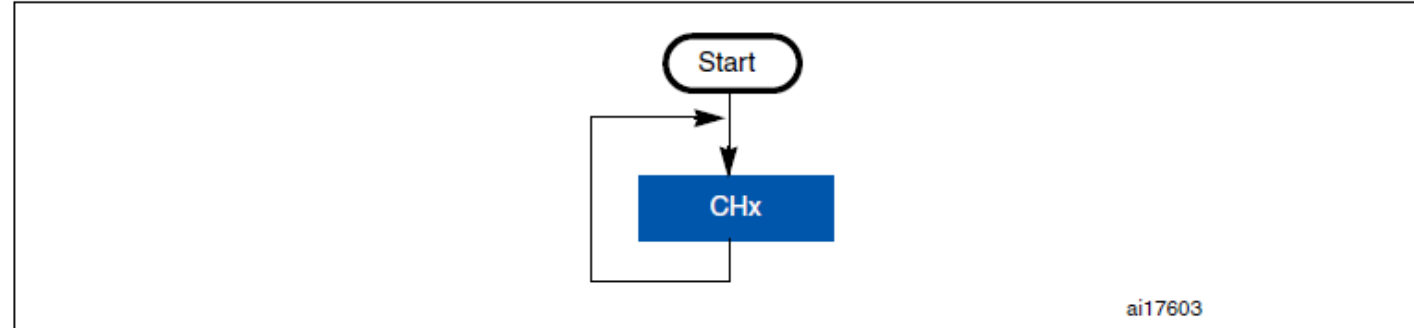


Figure 6. Injected conversion mode

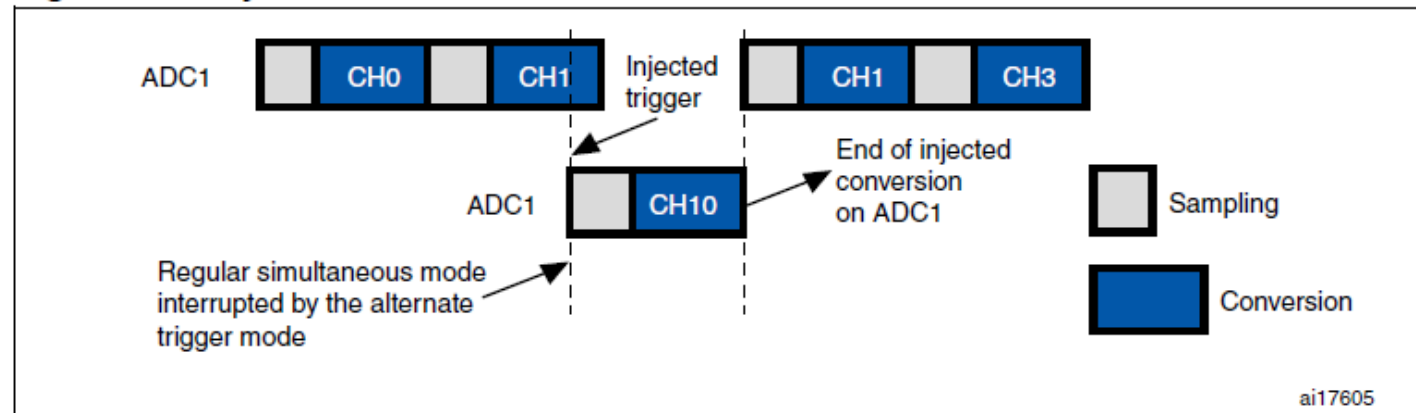


π

ADC Block Diagram

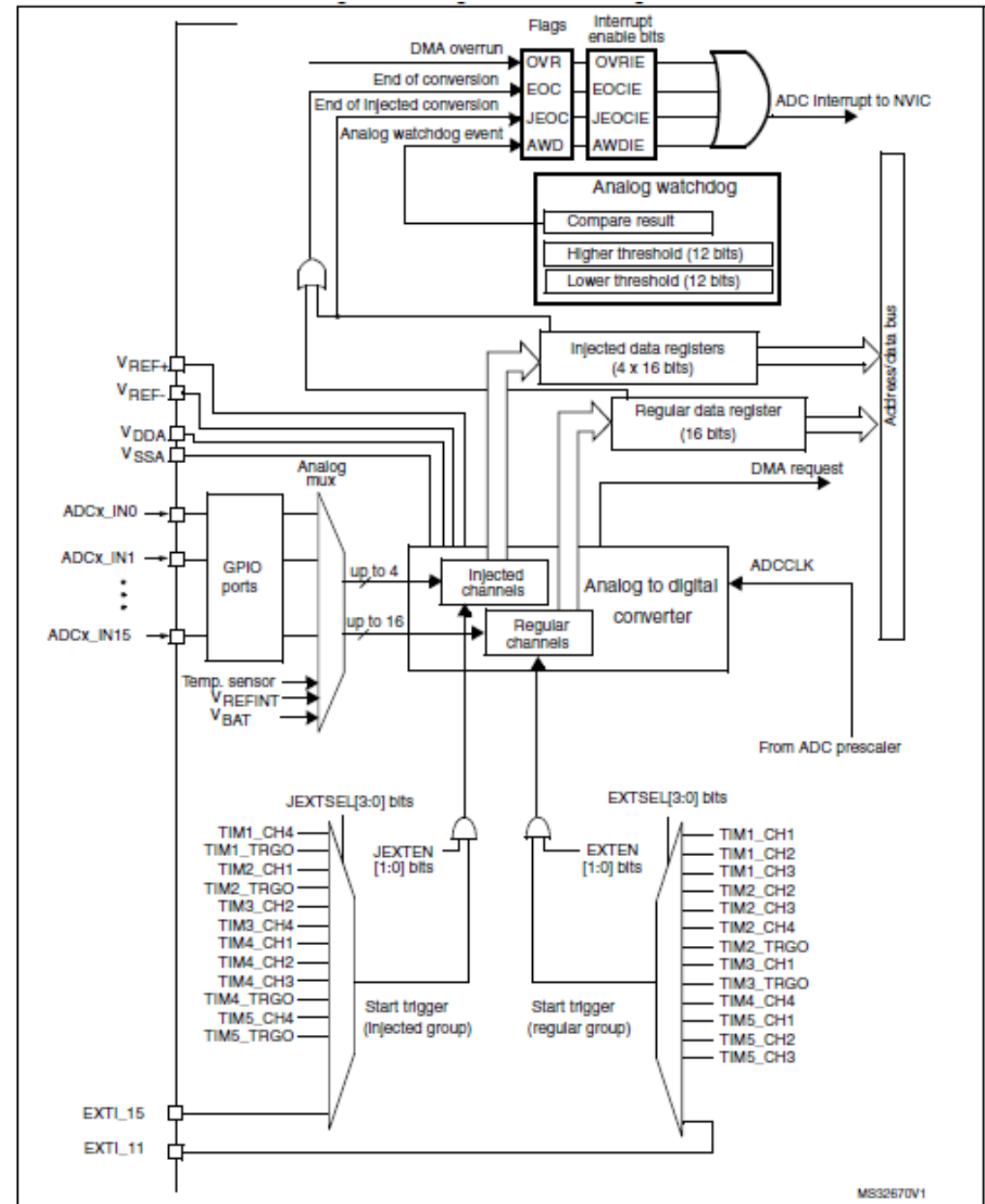

ADC Timing Diagram

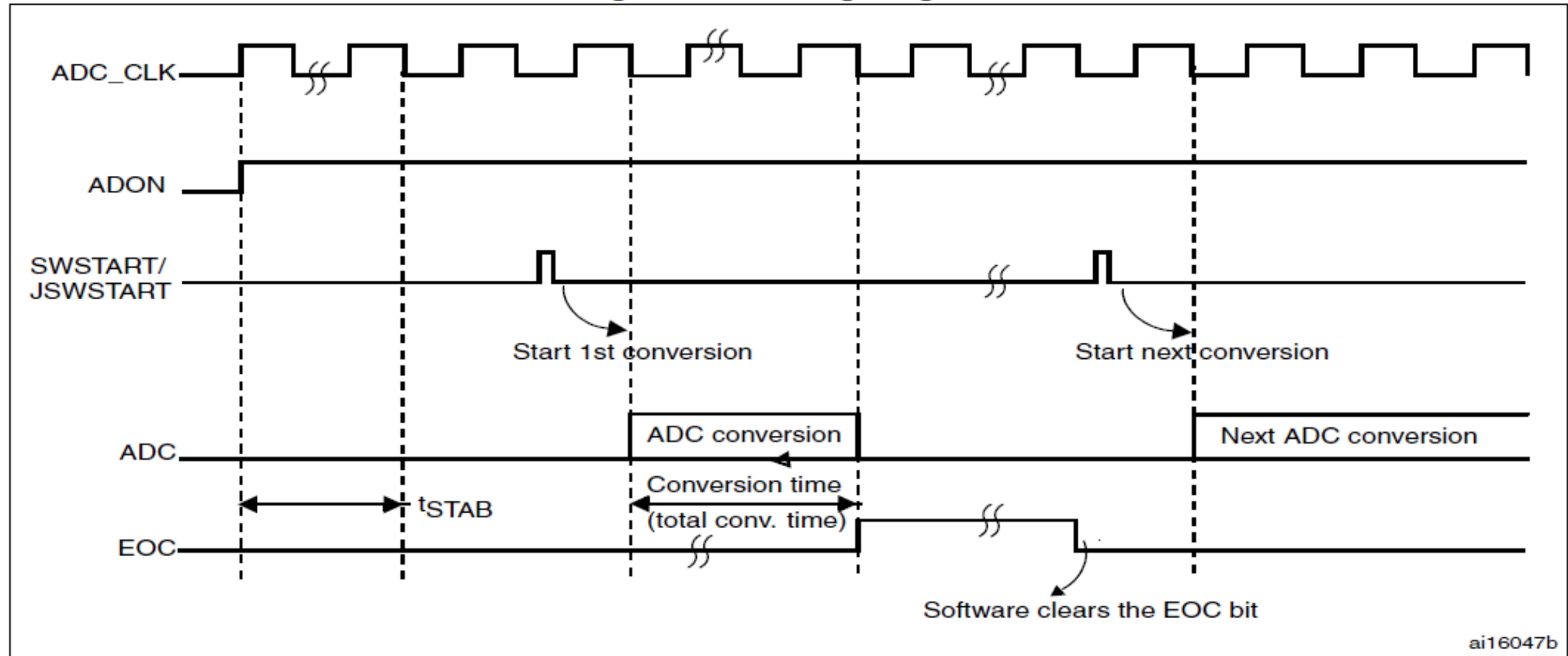

Data Alignment

Figure 35. Right alignment of 12-bit data

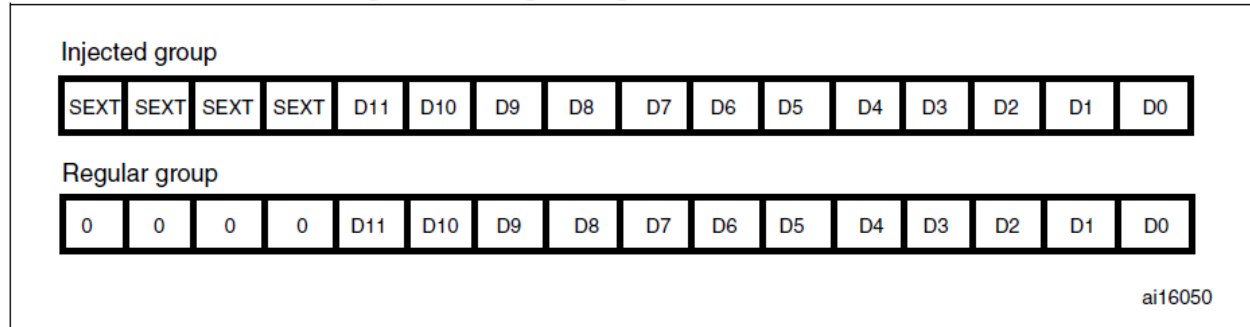


Figure 36. Left alignment of 12-bit data


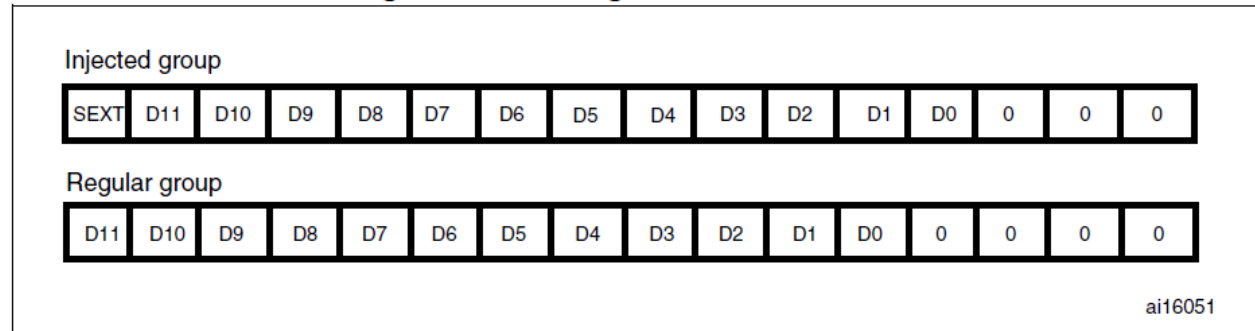


Figure 37. Left alignment of 6-bit data

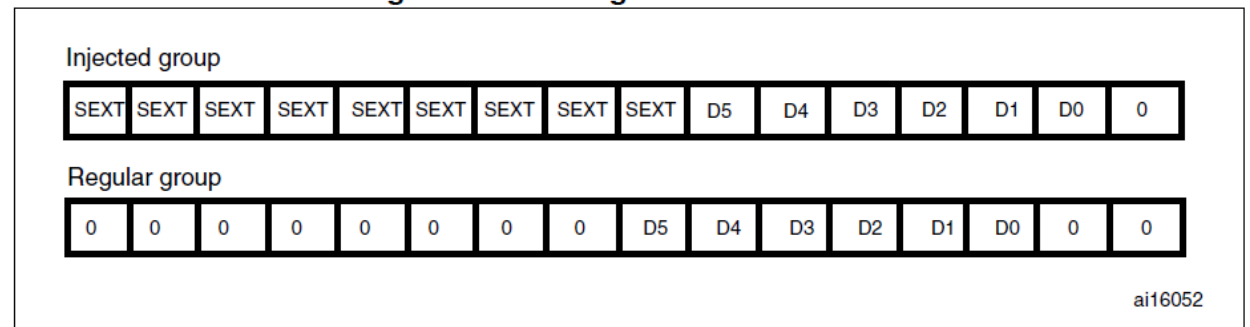

11.12.14 ADC regular data register (ADC_DR)

Address offset: 0x4C

Reset value: 0x0000 0000

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16
Reserved															
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
DATA[15:0]															
r	r	r	r	r	r	r	r	r	r	r	r	r	r	r	r

Bits 31:16 Reserved, must be kept at reset value.

Bits 15:0 **DATA[15:0]**: Regular data

These bits are read-only. They contain the conversion result from the regular channels. The data are left- or right-aligned as shown in [Figure 35](#) and [Figure 36](#).

```
volatile uint32_t adc_val = 0;
```

```
HAL_ADC_Start(&hadc1);
```




```
while (1){  
    while ( HAL_ADC_PollForConversion(&hadc1, 100) != HAL_OK ){}  
    adc_val = HAL_ADC_GetValue(&hadc1);  
}
```

ADC Configuration


The screenshot shows the 'Parameter Settings' tab in STM32CubeMX. A red circle with the number '3' is over the 'Parameter Settings' header. Below it, a search bar and navigation arrows are visible. The 'ADC_Settings' section is expanded, showing a list of parameters. The 'Continuous Conversion Mode' is highlighted with a red circle and the number '4'. Other parameters shown include Clock Prescaler (PCLK2 divided by 4), Resolution (12 bits), Data Alignment (Right alignment), Scan Conversion Mode (Disabled), Discontinuous Conversion Mode (Disabled), DMA Continuous Requests (Disabled), and End Of Conversion Selection (EOC flag at the end of single channel conversion).

Pin number					Pin name (function after reset) ⁽¹⁾	Pin type	I/O structure	Notes	Alternate functions	Additional functions
UQFN48	LQFP64	WL CSP49	LQFP100	UFBGA100L						
-	24	-	33	K5	PC4	I/O	FT	-	EVENTOUT	ADC1_14
-	25	-	34	L5	PC5	I/O	FT	-	EVENTOUT	ADC1_15
18	26	G5	35	M5	PB0	I/O	FT	-	TIM1_CH2N, TIM3_CH3, SPI5_SCK/I2S5_CK, EVENTOUT	ADC1_8
19	27	G4	36	M6	PB1	I/O	FT	-	TIM1_CH3N, TIM3_CH4, SPI5_NSS/I2S5_WS, EVENTOUT	ADC1_9

Potentiometer as Voltage Divider

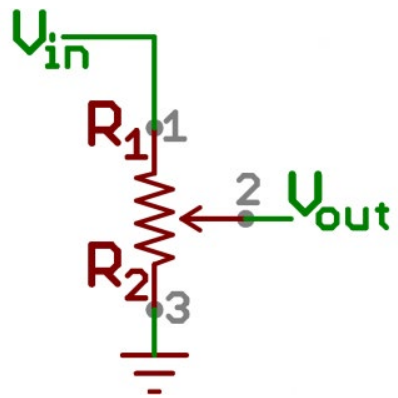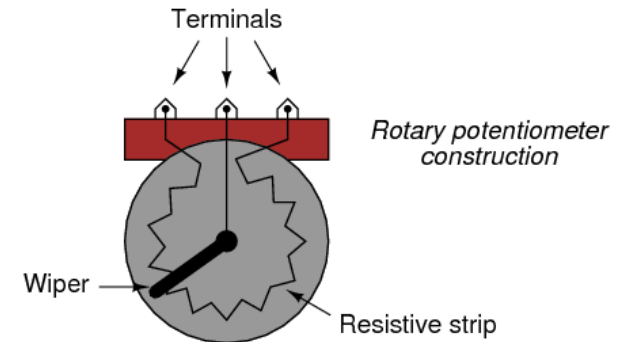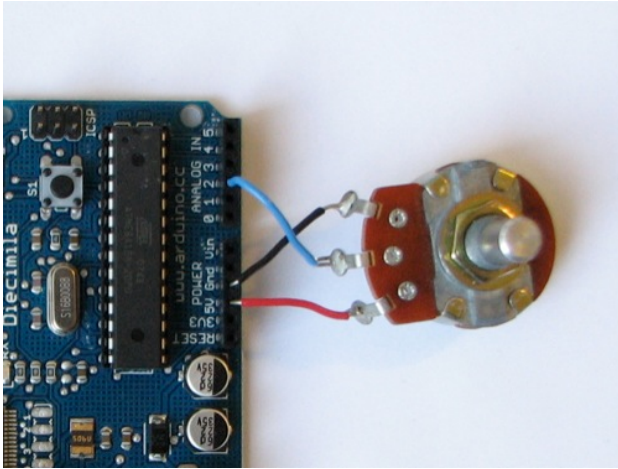

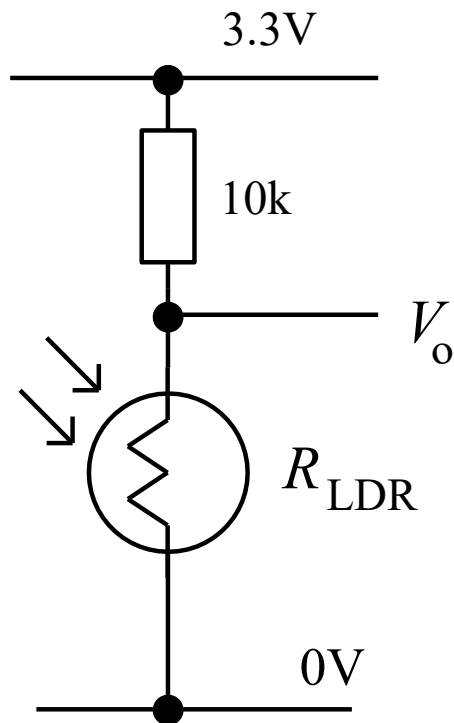Simple Analog Sensors : the Light Dependent Resistor




- LDR is made from semiconductor material.
- the brighter the light, the more electrons are released
- Released electrons are available to conduct electricity; the resistance falls
- Remove the light, electrons are back into their place; the resistance goes up again.



Illumination (lux)	$R_{LDR} (\Omega)$	V_o
Dark	$\geq 1.0 \text{ M}$	$\geq 3.27 \text{ V}$
10	9k	1.56 V
1,000	400	0.13 V

Integrated Circuit Temperature Sensor

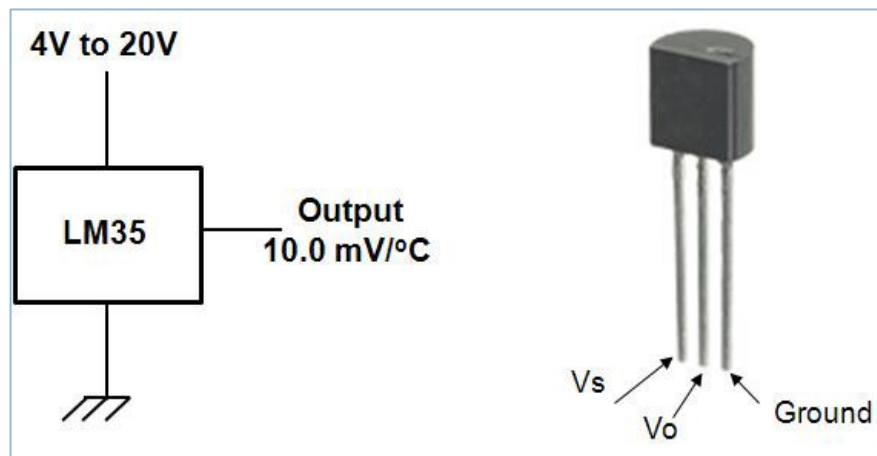- Semiconductor action is highly dependent on temperature
- LM35 has an output of 10 mV/°C
- Up to 110 °C



Summary

- Many applications using Analog voltage as input to MCU
- ADC converts analog signal to n bit digital code
- Keywords: input range, resolution, sampling rate and conversion time
- Nyquist's sampling theorem : The sampling frequency must be at least twice of the highest frequency analog input.
- ADC Data can be further processed, and displayed or stored.
- Numerous sensors have an analog output; can be directly connected to MCU ADC input.